

Stage 1 Design

Setting $I_B \approx 6 \mu A$

$$I_C = I_E = \beta I_B = (160)(6 \mu A) = 960 \mu A$$

$$I_{B1} = 6 \mu A$$

$$I_{C1}, I_{E1} \approx 960 \mu A$$

$$\beta = 160$$

Resistances

Approximate: $\beta R_E \geq 10 R_Z \rightarrow$ Choosing R_E to be 680

$$R_Z \leq 10.88 k\Omega \rightarrow \text{Selecting } R_Z = 10 k\Omega$$

$$R_E = 680$$

R_C :

$$V_C = V_{CC} - I_C(R_C + R_E)$$

$$4.5 V = 9 V - (960 \mu A)(R_C + 680) \rightarrow \left(\frac{4.5}{960 \mu A} \right) - 680 = R_C$$

$$R_C = 4087.5$$

$$\rightarrow 4.7 k\Omega \text{ or } 3.3 k\Omega$$

$$R_1: V_B = V_{CC} \left(\frac{R_Z}{R_1 + R_Z} \right)$$

$$1.35 V = 9 V \left(\frac{10.88 k}{10.88 k + R_1} \right)$$

$$\rightarrow R_1 = 61653.3 \Omega \rightarrow 47 k \text{ or } 68 k$$

$$\rightarrow I_E = \frac{V_E}{R_E}$$

$$\rightarrow V_E = (960 \mu A)(680) = 652.8 mV$$

$$V_B = V_E + 0.7$$

$$V_B = 1.35 V$$

SIMULATED

R_1	47k	$I_B(DC) = 8.63 \mu A$	\times Increase R_1 / Decrease R_Z
R_Z	10k	$V_B(DC) = 1.51 V$	$\rightarrow 68k$
R_C	3.3k	$I_C(DC) = 1.22 mA$	\downarrow controlling @ 10k
R_E	680	$V_C(DC) = 4.46 V$	\rightarrow increase R_C / Decrease R_E (≥ 625)

$$\rightarrow \frac{4.7k}{6.8k}$$

$$R_E = 625$$

✓ Simulated

R_1	68k	$I_B(DC) = 5.08 \mu A$
R_Z	10k	$V_B(DC) = 1.11 V$
R_C	6.8k	$I_C(DC) = 665 \mu A$
R_E	680	$V_C(DC) = 4.48 V$

Stage 1 DC parameters

$$R_1 = 68k\Omega \quad R_2 = 10k\Omega \quad R_C = 6.8k\Omega \quad R_E = 680\Omega$$

Approximate test, $\beta = 160$

$$\beta(R_E) \geq 10R_2 \quad \checkmark$$

$$(160)(680\Omega) \geq 10(10k) \rightarrow 108k \geq 100k$$

$$V_B = 9V \left(\frac{10k}{68k + 10k} \right) \approx 1.15V_B$$

$$V_E = V_B - V_{BE} = 1.15V - 0.7V = 450mV = V_E$$

$$I_E = V_E / R_E = \frac{450mV}{680\Omega} = 661.76\mu A \quad I_E$$

$$I_E \approx I_C, \quad I_C \approx 661.76\mu A$$

$$V_C = V_{CC} - I_C(R_C + R_E)$$

$$= 9V - 661.76\mu A(6.8k + 680)$$

$$I_B = \frac{I_C}{\beta} = \frac{661.76\mu A}{160}$$

$$I_B = 4.14\mu A$$

$$V_C \approx 4.05V$$

No Load
SIMULATED DC PARAMETERS

$$\begin{aligned} V_{B1} &= 1.15V \\ V_{C1} &= 4.05V \\ V_{E1} &= 450mV \\ I_{B1} &= 4.14\mu A \\ I_{C1} &= 661\mu A \\ I_{E1} &= 661\mu A \end{aligned}$$

$$\begin{aligned} V_{B1} &= 1.11V \\ V_{C1} &= 4.48V \\ V_{E1} &= 456mV \\ I_{B1} &= 5.08\mu A \\ I_{C1} &= 665\mu A \\ I_{E1} &= 670\mu A \end{aligned}$$

$$\begin{aligned} V_{B2} &= 1.11V \\ V_{C2} &= 4.48V \\ V_{E2} &= 456mV \\ I_{B2} &= 5.08\mu A \\ I_{C2} &= 665\mu A \\ I_{E2} &= 670\mu A \end{aligned}$$

$$A_{V, NL} = \frac{R_C}{-R_E}$$

$$= -\frac{6.8k}{680} \approx -10$$

$$\text{Simulated: } \frac{V_O}{V_i} = \frac{110.019mV}{-11.764mV}$$

$$A_{V_O, 1} \rightarrow -9.35V/V$$

Stage 2 DC Parameters

→ Copied Stage 1 for Stage 2

→ All Design requirements verified to be within spec using Multisim for Q1 + Q2

$$A_{V_O, 2} = -\frac{6.8k}{680} = -10V/V$$

$$\text{Sim: } -9.31V/V$$

Gain (2-stage)

Stage 1

$$R_{in} = R_1 \parallel R_2 \parallel \beta(r_e + R_E) \rightarrow r_e = \frac{26mV}{661\mu A} = 39.33\Omega$$

$$= 68k \parallel 10k \parallel 160(39.33 + 680)$$

$$R_{in,1} = 8.1k\Omega$$

$$R_{out,1} \approx R_C = 6.8k\Omega$$

Stage 2

$$R_{in} = R_3 \parallel R_4 \parallel \beta(r_{e2} + R_{E2}) \rightarrow r_e = \frac{26mV}{2.04mA} = 12.75\Omega$$

$$= 68k \parallel 10k \parallel \beta(12.75 + 680)$$

$$R_{in,2} = 7.18k\Omega$$

$$R_{out,2} = R_{C2} = 6.8k\Omega$$

$$A_{vo,1} = \frac{-R_C}{R_E} = \frac{-6.8k}{680} = -10V/V$$

$$A_{v,1} = \frac{R_C \parallel R_L}{-R_E} = \frac{6.8k \parallel 7.18k\Omega}{-680} = -5.14V/V$$

$$A_{vo,2} = \frac{-R_C}{R_E} = -10V/V$$

$$A_{vT,NL} = A_{v,1} A_{v,2} = (-5.14)(-10) = 51.4V/V$$

$$A_{VT} = \left(\frac{R_L}{R_L + Z_o} \right) A_{vT,NL} = \left(\frac{100k}{100k + 6.8k} \right) 51.4 = 48.13V/V$$

Too high. Decrease R_3
 & decrease R_4 to
 lower gain while maintaining
 $\beta R_{E2} \geq 10R_4$

→ Through simulation,
 determined decrease by 2
 standard R_{sig} values

$$\rightarrow R_3 = 33k \parallel R_4 = 4.7k$$

Gain (2-stage) cont.

Stage 2, adjusted

$$R_{in} = 33k \parallel 4.7k \parallel (160 \cdot (12.75 + 680))$$

$$R_{in} = 3.97 k\Omega$$

$$R_{out} = 6.8 k\Omega$$

Stage 1 (unchanged)

$$R_{in} = 8.1 k\Omega$$

$$R_{out} = 6.8 k\Omega$$

$$A_{v,1} = \frac{-6.8k \parallel 3.97k}{680} = -3.69 V/V$$

$$A_{v0,2} = \frac{-6.8k}{680} = -10 V/V$$

$$A_{v,TL} = (-3.69)(-10) = 36.9 V/V$$

$$A_{vT} = \left(\frac{100k}{100k + 6.8k} \right) 36.9 = 34.55 V/V$$

$$\text{Measured: } \frac{V_o}{V_i} = \frac{715mV}{23.7mV} = 30.2 V/V$$

Cutoff analysis

3x poles, formed by C_{c1} , C_{c2} , C_{c3}

$$100 Hz = \frac{1}{2\pi(R_{in,1})(C_{c1})} \rightarrow C_{c1} = \frac{1}{2\pi(100)(8.1k)} \approx 196 nF$$

$$100 Hz = \frac{1}{2\pi(R_{c1})(C_{c2})} \rightarrow C_{c2} = \frac{1}{2\pi(100)(6.8k)} \approx 234 nF$$

$$100 Hz = \frac{1}{2\pi(R_{c2})(C_{c3})} \rightarrow C_{c3} = \frac{1}{2\pi(100)(6.8k)} \approx 234 nF$$

0.22 μF standard

$$\frac{1}{2\pi(6.8k)(.22\mu F)} = 106.39 Hz \leftarrow \omega_{p3}$$

$$\text{Choosing } 1\mu F \rightarrow \frac{1}{2\pi(6.8k)(1\mu F)} \approx 23.41 Hz \omega_{p2}$$

$$f_L \approx 106 Hz$$

→ using .22 μF standard cap

$$\text{Choosing } 1\mu F \rightarrow \frac{1}{2\pi(8.1k)(1\mu F)} \approx 20 Hz \omega_{p1}$$