

Stage 2 Design

→ Designed with $I_{BZ} = \text{max}$,
lowers gain A_{V2} to insert
clipping stage before

$$\beta = 160, R_E = 680\Omega, R_Z = 10k\Omega$$

→ $10.88 k\Omega$ exact

$$I_{BZ} \approx 15 \mu A$$

$$I_C = \beta I_B = (160)(15 \mu A)$$

$$I_F = 2.4 \text{ mA}$$

$$I_C \approx I_E \approx 2.4 \text{ mA}$$

$$V_C = 4.5V = 9V - 2.4 \text{ mA}(R_C + 680)$$

$$\left(\frac{-4.5V}{-2.4 \text{ mA}} \right) - 680 = R_C = 1195 \Omega$$

Choose 1k or 1.5k

R_i :

$$\frac{1}{2.332} = 9V \left(\frac{10.88k}{10.88k + R_i} \right)$$

$$R_i = 31110 \Omega$$

$\Rightarrow 33k$

$$I_E = V_E / R_E$$

$$2.4 \text{ mA} (680) = V_E = 1.632 \text{ V}$$

$$V_B = V_E + 0.7$$

$$V_B = 2.332 \text{ V}$$

Simulated:

R_i	33k	I_B	12.6 μA
R_Z	10k	V_B	2V
R_C	1k	I_C	1.92mA
R_E	680	V_C	7.08V

→ increase R_C / Decrease $R_E (\geq 625)$

1.5k
2.2k

R_i	33k	I_B	12.9 μA
R_Z	10k	V_B	1.99V
R_C	2.2k	I_C	1.92mA
R_E	680	V_C	4.78V

Stage 2 DC param.

For Adding Clipping

$$R_1 = 33k, R_2 = 10k, R_C = 2.2k, R_E = 680$$

$$\beta R_E \geq 10R_2$$

$$(160)(680) \geq 10(10k) \rightarrow 108k \geq 100k \checkmark$$

$$V_B = 9V \left(\frac{10k}{43k} \right) = 2.09V = V_B$$

$$V_E = V_B - V_{BE} = 2.09 - 0.7 = 1.39V = V_E$$

$$I_E = V_E / R_E = 1.39V / 680\Omega = 2.04mA = I_E$$

$$V_C = V_{CC} - I_C(R_C + R_E)$$

$$= 9 - 2.04mA(2.2k + 680)$$

$$V_C = 2.09V$$

$$I_E \approx I_C, I_C \approx 2.04mA$$

$$I_B = \frac{I_C}{\beta} = \frac{2.04mA}{160} = 15\mu A \checkmark$$

$$I_B = 15\mu A$$

V_B	2.09V
V_C	2.09V
V_E	1.39V
I_B	15nA
I_C	2.04mA
I_E	2.04mA

simulated	
V_B	1.99V
V_C	1.92V
V_E	1.31V
I_B	12.9nA
I_C	1.92mA
I_E	1.93mA

$$A_{v,NL} = \frac{R_C}{R_E}$$

$$= -2.2k \approx -3.2V/V$$

$$\text{Simulated } \frac{V_o}{V_i} = \frac{18.112mV}{-5.906mV}$$

$$A_{v,2}$$

$$= -3.1V/V$$

Gain Parameters (modified)

Stage 1

$$r_e = \frac{26mV}{661\mu A} = 39.33 \Omega$$

$$Z_i = R_1 || R_2 || \beta(r_e + R_E)$$

$$= 68k || 10k || 160(39.33 + 680)$$

$$Z_i = 8.1 k\Omega$$

$$A_{v1} = -\frac{R_C || R_L}{R_E}$$

$$A_{v1} = \frac{6.8k || 2.2k}{-680}$$

$$A_{v1} = -5.14 V/V$$

$$Z_o \approx R_C = 6.8k\Omega$$

Stage 2

$$r_e = \frac{26mV}{2.04mA} = 12.75 \Omega$$

$$Z_i = R_1 || R_2 || \beta(r_e + R_E)$$

$$= 33k || 10k || 160(12.75 + 680)$$

$$Z_i = 7.18 k\Omega$$

$$A_{v2,NL} = -\frac{R_C}{R_E} = -\frac{2.2k}{680}$$

$$Z_o \approx R_C = 2.2 k\Omega$$

$$A_{v2} = -3.24$$

Total

$$A_{vT(NL)} = (A_{v1}) \cdot (A_{v2(NL)}, z)$$

$$A_{vT,NL} = (-5.14)(-3.24) = 16.65 V/V$$

$$A_{vT,L} = \left(\frac{100k}{100k + 2.2k} \right) 16.65 = 16.29 V/V$$